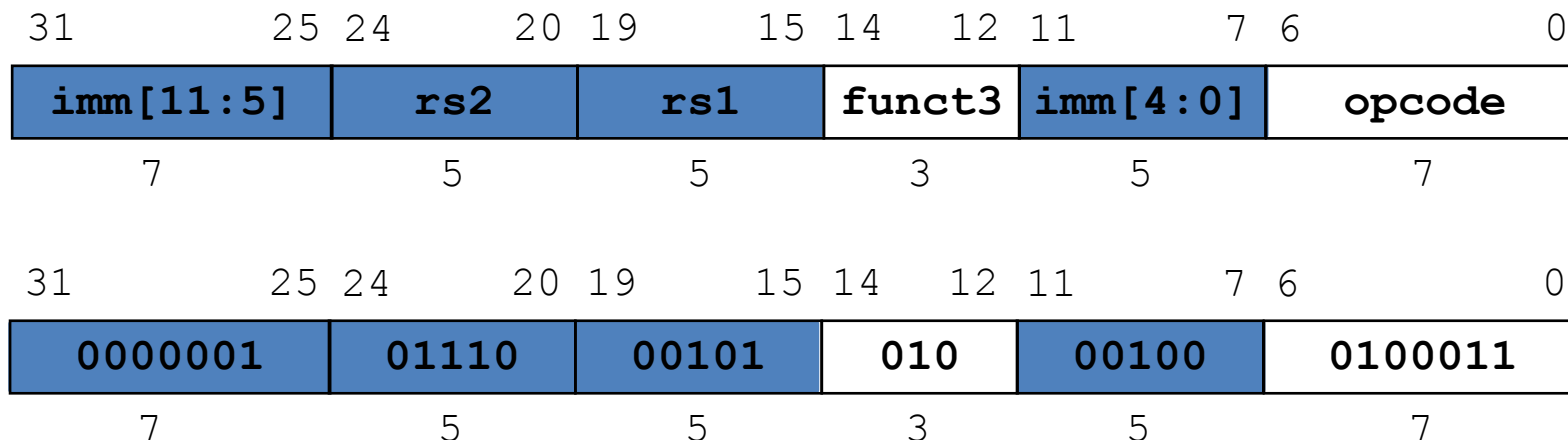


Intro to Digital Systems

Store Format Example


sw x14, 36(x5)



36 = 0b


01	00100
----	-------

Levels of Representation/Interpretation

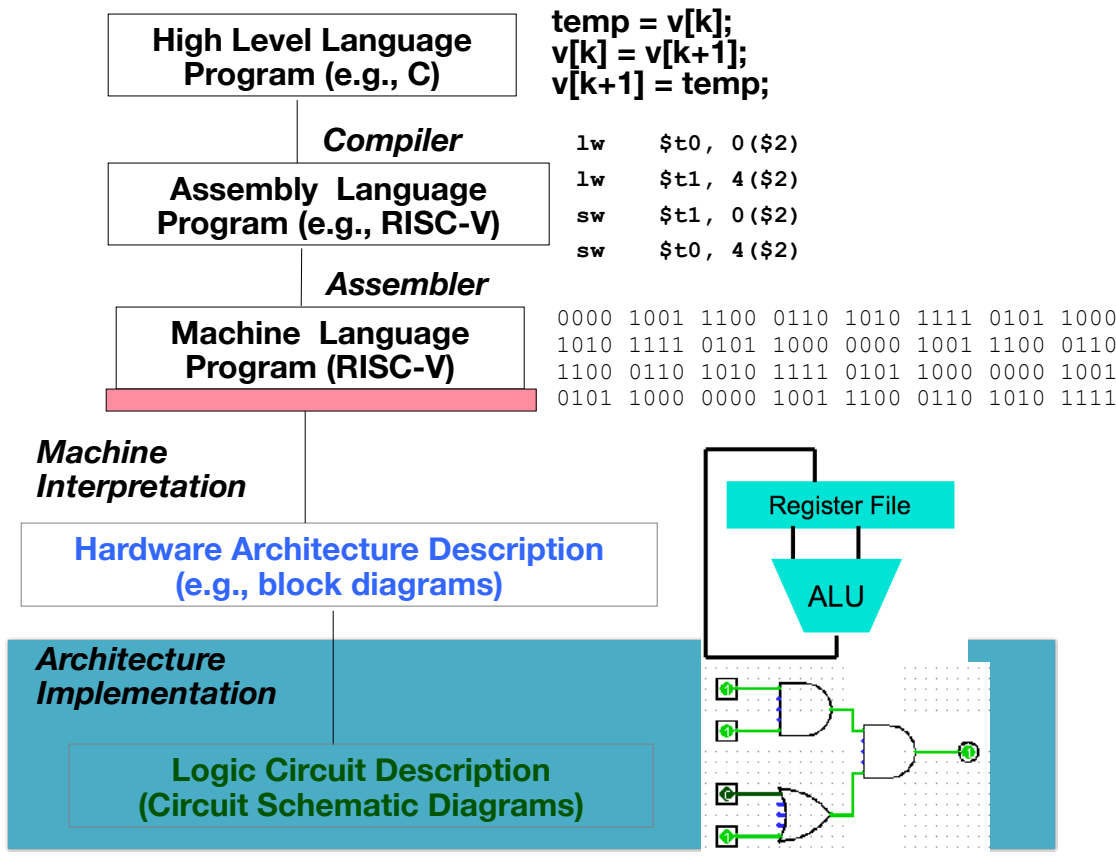

Digital Systems

 - Digital
 - All values are discrete
 - A value can be on (1) or off (0)
- Analog
 - Have a continuous range of values




Logic Gates

Logic Gates

- The building block of digital circuits
- Perform logic operations
 - AND
 - OR
 - XOR
 - NOT
 - NAND
 - NOR
 - XNOR

AND


A	B	out
0	0	0
0	1	0
1	0	0
1	1	1

 

`out = A & B`
 ↑
 C syntax

OR


A	B	out
0	0	0
0	1	1
1	0	1
1	1	1

 

`out = A | B`
 ↑
 C syntax

XOR

A	B	out
0	0	0
0	1	1
1	0	1
1	1	0

 


$$\text{out} = A \wedge B$$

↑
C syntax

NOT


A	out
0	1
1	0

 

$\text{out} = \sim A$
 ↑
 C syntax

NAND

A	B	out
0	0	1
0	1	1
1	0	1
1	1	0

 


$$\text{out} = \sim (A \ \& \ B)$$

C syntax

NOR

A	B	out
0	0	1
0	1	0
1	0	0
1	1	0

 


$$\text{out} = \sim (A \mid B)$$

C syntax

XNOR

A	B	out
0	0	1
0	1	0
1	0	0
1	1	1

 

$$\text{out} = \sim (A \wedge B)$$

C syntax


Logic operations on 32 bit numbers

$$C = A \ \& \ B$$

$$A = A_{31} \ A_{30} \ A_{29} \ \dots \ A_0$$


$$B = B_{31} \ B_{30} \ B_{29} \ \dots \ B_0$$
 
$$C = C_{31} \ C_{30} \ C_{29} \ \dots \ C_0$$



Connecting Logic Gates

$$\text{out} = (A \ \& \ B) \ | \ C$$

 

(A, B, and C are one bit each)

Boolean Algebra

Boolean Algebra

- A branch of algebra in which
 - The operands can only be 0 or 1
 - The basic operations are AND, OR, and NOT
 - (NAND, NOR, XOR, and XNOR can be created with a combination of the above operations)


Boolean Notation

Operation	C Notation	Boolean Notation
A AND B	A & B	AB
A OR B	A B	A + B
NOT A	~A	\bar{A}

Boolean Algebra


C notation: **out** = (**A** & **B**) | **C**

 Boolean notation: **out** = **AB** + **C**



Boolean Equation -> Truth Table


$$\text{out} = AB + C$$

 

A	B	C	out
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Boolean Equation -> Logic Gate Diagram

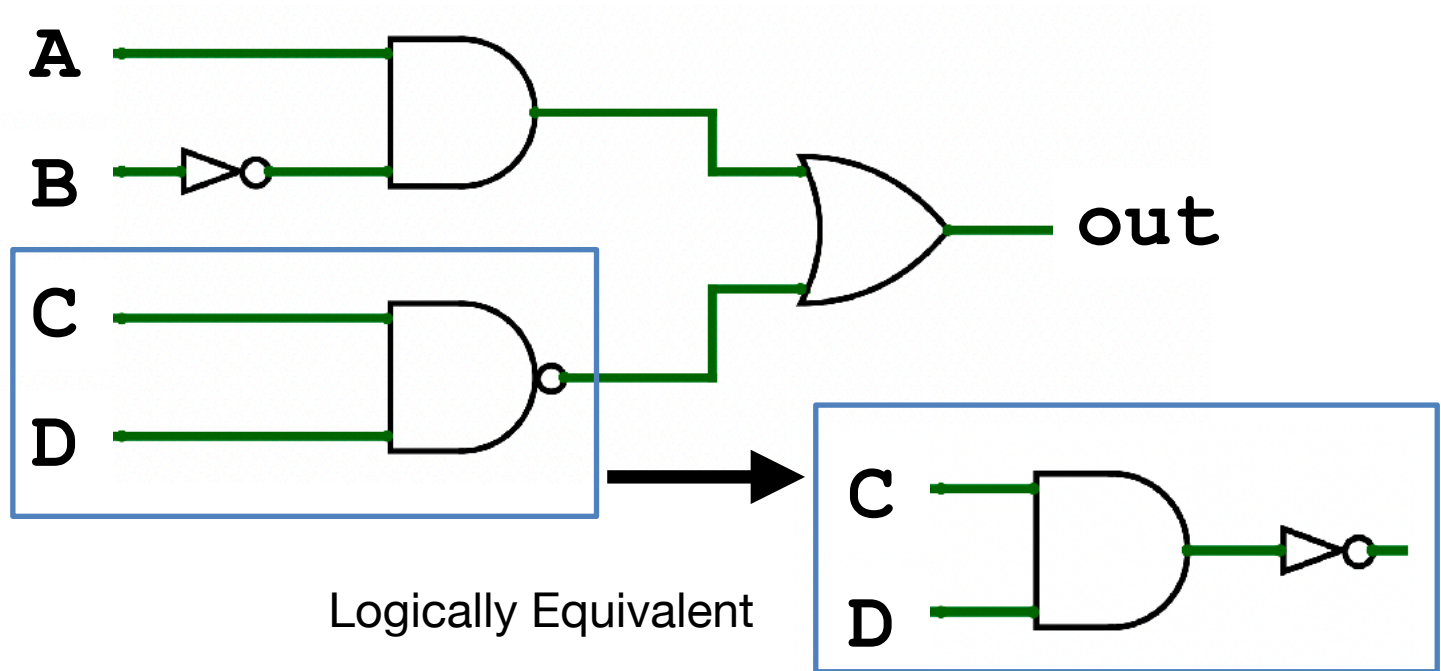
$$\text{out} = A\bar{B} + \overline{CD}$$




Truth Table to Circuit Diagram

A	B	C	out
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	0
 
$$\text{out} = \bar{A}\bar{B}C + A\bar{B}\bar{C}$$



Logically
Equivalent

 

How to Make XOR with AND and OR

A	B	out
0	0	0
0	1	1
1	0	1
1	1	0

$$\text{out} = \bar{A}B + A\bar{B}$$

How to Make XNOR with AND and OR

A	B	out
0	0	1
0	1	0
1	0	0
1	1	1

$$\text{out} = \overline{A}\overline{B} + AB$$

Laws of Boolean Algebra

Complementary

$$A\bar{A} = 0$$

$$A + \bar{A} = 1$$

Laws of Boolean Algebra

Laws of 0's and 1's

$$A0 = 0$$

$$A + 1 = 1$$

Laws of Boolean Algebra

Identities

$$A1 = A$$

$$A + 0 = A$$

Laws of Boolean Algebra

Idempotent

$$AA = A$$

$$A + A = A$$

Commutativity

$$AB = BA$$

$$A + B = B + A$$

Associativity

$$(AB)C = A(BC)$$

$$(A + B) + C = A + (B + C)$$

Distribution

$$A (B + C) = AB + AC$$

$$A + BC = (A + B) (A + C)$$

Uniting Theorem

$$AB + A = A$$

$$(A + B)A = A$$

Uniting Theorem #2

$$\overline{A}B + A = A + B$$

Uniting Theorem #2

$$(\overline{A} + B)A = AB$$

Laws of Boolean Algebra

DeMorgan's Law


$$\overline{AB} = (\overline{A} + \overline{B})$$

Laws of Boolean Algebra

DeMorgan's Law

$$\overline{(A + B)} = \overline{A} \overline{B}$$

 Using Boolean Algebra to Simplify Circuits




$$\text{out} = AB + B + C$$

$$\text{out} = B(A + 1) + C$$


$$\text{out} = B + C$$

Using Boolean Algebra to Simplify Circuits

$$\text{out} = AB + B + C$$

 


$$\text{out} = B + C$$

 

Recall: Boolean Equation -> Truth Table

$$\text{out} = AB + C$$

 

1. Determine when each product will be true
2. Place a one in the corresponding rows
3. Place a zero in the remaining rows

A	B	C	out
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Sum of Products

- When two or more products (AND) are summed (OR) together

$$\text{out} = AB + AC$$

~~$$\text{out} = A(B + C)$$~~

- When the equation is written in this form, it is easier to convert it to a truth table

Sum of Products

$$\text{out} = (A + B) (A + C)$$

$$\text{out} = AA + AC + AB + BC$$

$$\text{out} = A + AC + AB + BC$$

$$\text{out} = A(1 + C + B) + BC$$

$$\text{out} = A + BC$$

A	B	C	out
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

How to Build an Adder

Recall: Binary Addition

Carry out from the
second column /
Carry into the third
column

$$\begin{array}{r} 111 \\ + 101 \\ + 111 \\ \hline 100 \end{array}$$

Carry in to the
second column


Half Adder

- How to add two bits together using logic gates?



A	B	C _o	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

$$S = A \oplus B$$

$$C_o = AB$$

 

Half Adder Abstraction

  

Recall: Binary Addition

Carry out from the
second column /
Carry into the third
column

$$\begin{array}{r} 111 \\ + 101 \\ + 111 \\ \hline 100 \end{array}$$

Carry in to the
second column

Full Adder (single bit)

A	B	C _i	C _o	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

S is 1 when 1 or 3 of the bits are 1

$$S = A \oplus B \oplus C_i$$

Full Adder (single bit)

A	B	C _i	C _o	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$C_o = \bar{A}BC_i + A\bar{B}C_i + AB\bar{C}_i + ABC_i$$


$$C_o = C_i (\bar{A}B + A\bar{B}) + AB (\bar{C}_i + C_i)$$

$$C_o = C_i (A \oplus B) + AB$$



Full Adder

$$S = A \oplus B \oplus C_i$$


$$C_o = AB + C_i (A \oplus B)$$

 

Full Adder Abstraction

  

4-bit Adder

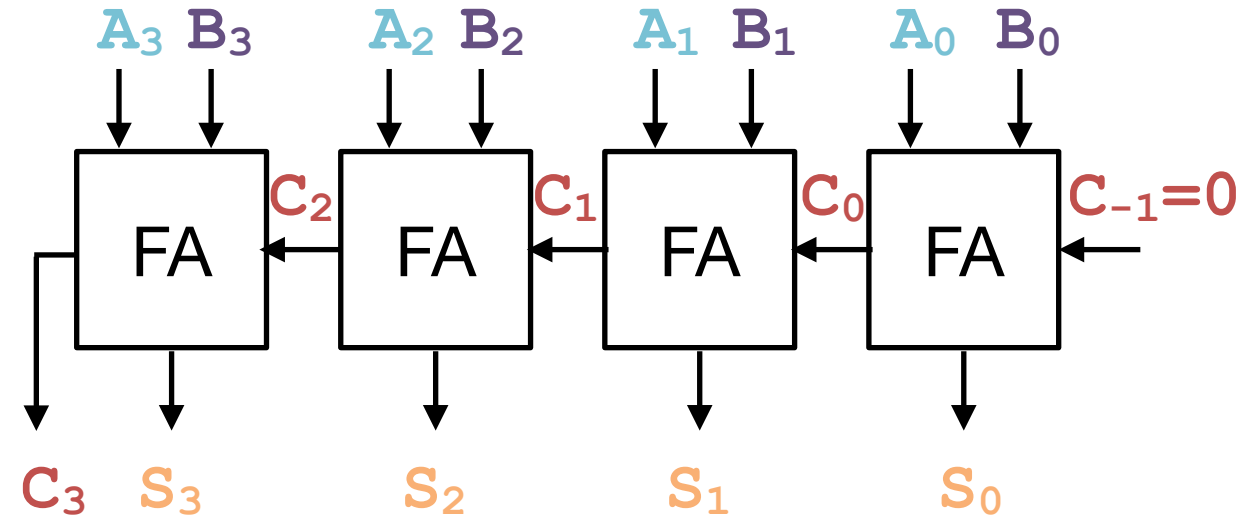

$$\begin{array}{rcccccc} C_3 & C_2 & C_1 & C_0 & C_{-1} = 0 & \\ A_3 & A_2 & A_1 & A_0 & & \\ B_3 & B_2 & B_1 & B_0 & & \\ \hline S_3 & S_2 & S_1 & S_0 & & \end{array}$$

Arithmetic Logic Unit

Arithmetic Logic Unit (ALU)

- Carries out arithmetic and logical operations on integer binary numbers


Recall: Logical AND on 32-bit Number

$$X = AB$$



$$A = A_{31} \ A_{30} \ A_{29} \ \dots \ A_0$$

$$B = B_{31} \ B_{30} \ B_{29} \ \dots \ B_0$$

 
$$X = X_{31} \ X_{30} \ X_{29} \ \dots \ X_0$$



Logical AND on 32-bit Number Abstraction

  


Arithmetic Logic Unit

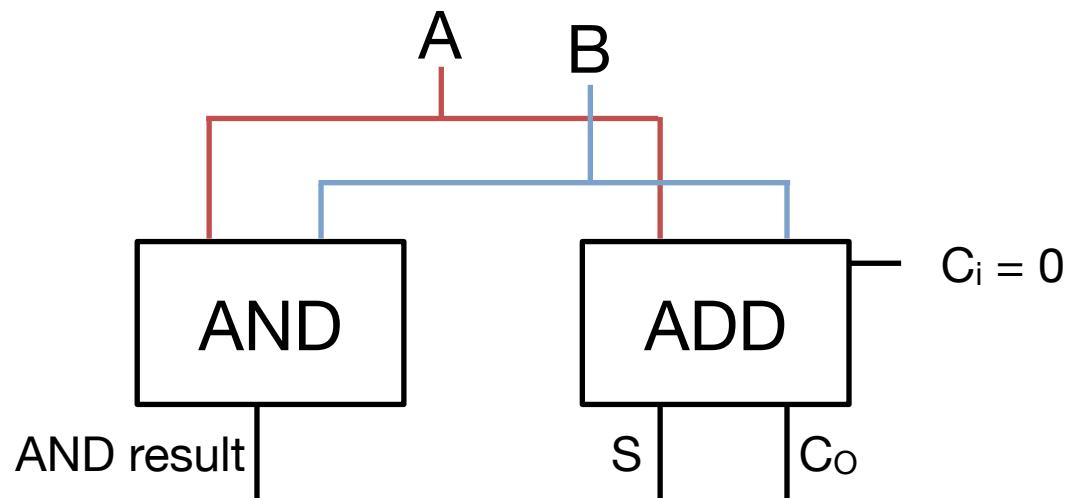

 
2:1 Multiplexors (Abstraction)

- Selects an input to propagate to the output




If select = 0, out = AND Result
If select = 1, out = ADD Result

Arithmetic Logic Unit

 

2:1 Mux Implementation

 


$$\text{out} = A\bar{S} + BS$$

2:1 Mux Implementation



Select

$$\text{out} = A\bar{S} + BS$$

 

Combinational Logic

- Everything that we have talked about so far is called combinational logic
- As soon as the inputs are available, the output starts being computed
- Output depends only on the current input
 - We'll see circuits whose outputs depend on more than the current input in the next lecture